

MADVLSI Miniproject 2  
Vienna Scheyer  
03/02/2021

github: [https://github.com/vscheyer/MADVLSI/tree/master/Mini\\_Project\\_2](https://github.com/vscheyer/MADVLSI/tree/master/Mini_Project_2)

For this project, I made a 4-bit shift register based on complementary set-reset logic (CSRL) flip-flop stages. This type of cell behaves in a similar way to a D flip-flop, but the CSRL is not ratioless. In other words, the transistor ratios affect the operation of the device. I based my design on Massimo Antonio Sivilotti's California Institute of Technology PhD thesis paper.<sup>1</sup> The strength ratio of importance is that of the pass transistors, which are  $M_8$  and  $M_9$  in my schematic as shown in Figure 1.

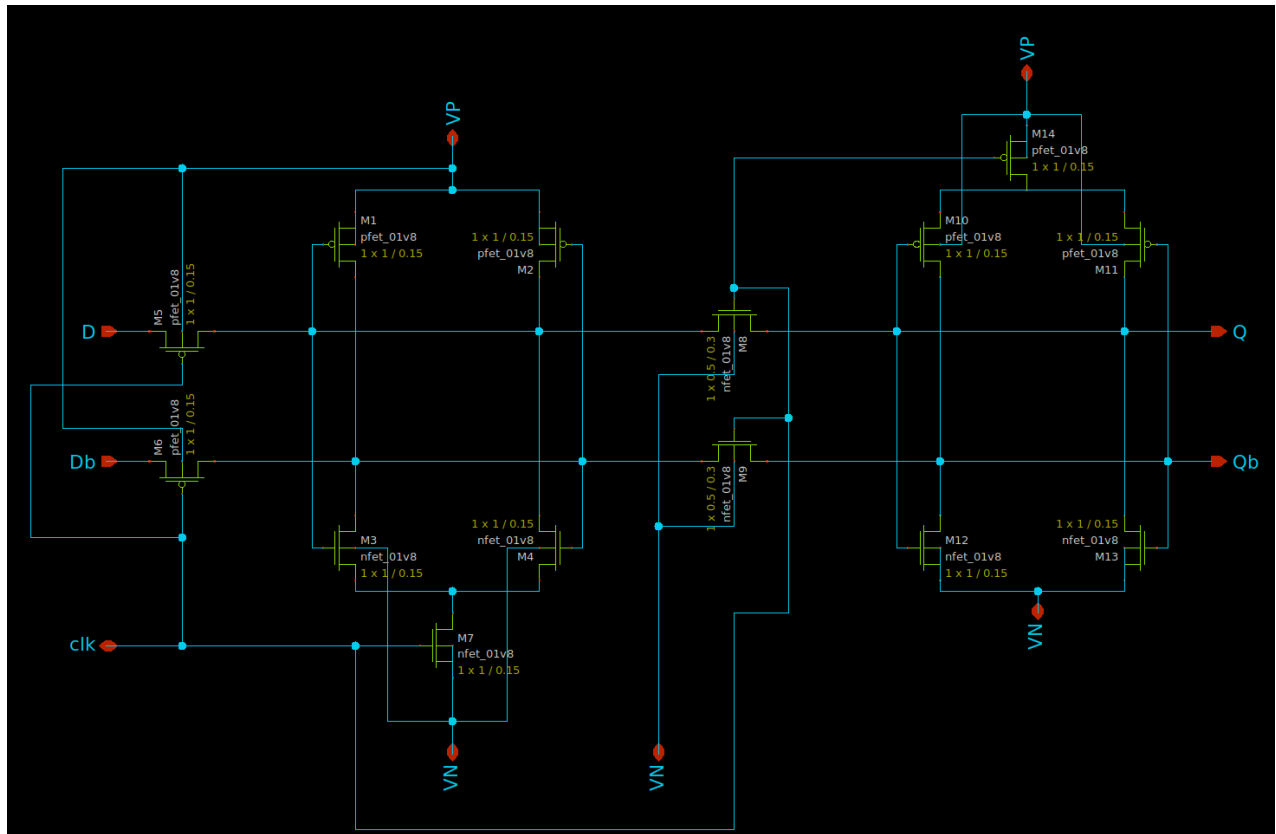


Figure 1: CSRL Schematic

It is desirable to achieve a strength ratio for the pass transistors such that the following ratio holds true:

$$\frac{\frac{W_{M7}}{L_{M7}}}{\frac{W_{M8}}{L_{M8}}} = 4$$

<sup>1</sup> <http://madvlsi.olin.edu/madvlsi/internal/Sivilotti91.pdf>

In this case,  $M_8$  is a pass transistor and  $M_7$  is another transistor in the circuit. The strength ratios of the  $M_8$  and  $M_9$  pass transistors should match. Since I started with all my transistors at  $W=1\text{ }\mu\text{m}$  and  $L=0.15\text{ }\mu\text{m}$ , I calculated that I could change the widths of  $M_8$  and  $M_9$  to  $0.25\text{ }\mu\text{m}$  to achieve the suggested ratio of 4. However, when I went to implement this in my layout I ran into a design rule violation that specified the transistors may have a minimum width of  $0.42\text{ }\mu\text{m}$ . I changed the lengths of the pass transistors to  $0.3\text{ }\mu\text{m}$  to account for this, and so my pass transistors proportionally then had a width of  $W=0.5\text{ }\mu\text{m}$ .

Figure 2 shows my CSRL layout. My CSRL has a cell width of  $4.75\text{ }\mu\text{m}$ .

 


Figure 2: CSRL layout. Cell width =  $4.75\text{ }\mu\text{m}$ .

Before moving on to the next step, I performed LVS on the CSRL cell to make sure those netlists matched. I checked that the transistor lengths and widths matched as well. Figure 3 shows the schematic I used to export a netlist for LVS. The output file from this LVS is in the *CSRL/lvs/* folder.

 


Figure 3: Top level schematic for exporting a CSRL netlist.

Next, I created a 4-bit shift register schematic by chaining together four CSRL latches. I also added an inverter to create the Db input from the D input. Figure 4 shows the shift register top level schematic that I used to export a netlist for LVS.

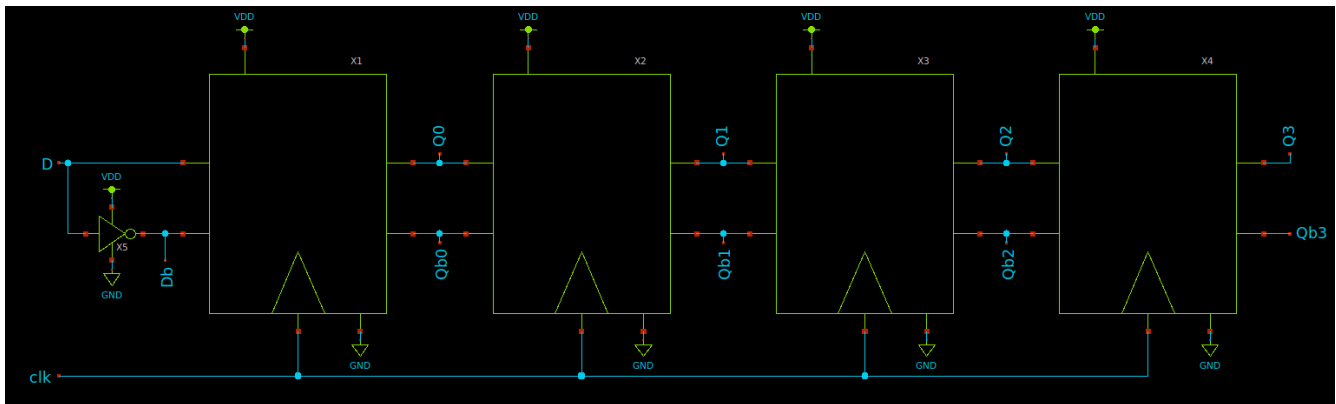


Figure 4: Top level schematic for exporting 4-bit shift register netlist.

I copied my shift register schematic over into a new file to create my transient simulation harness as shown in Figure 5.

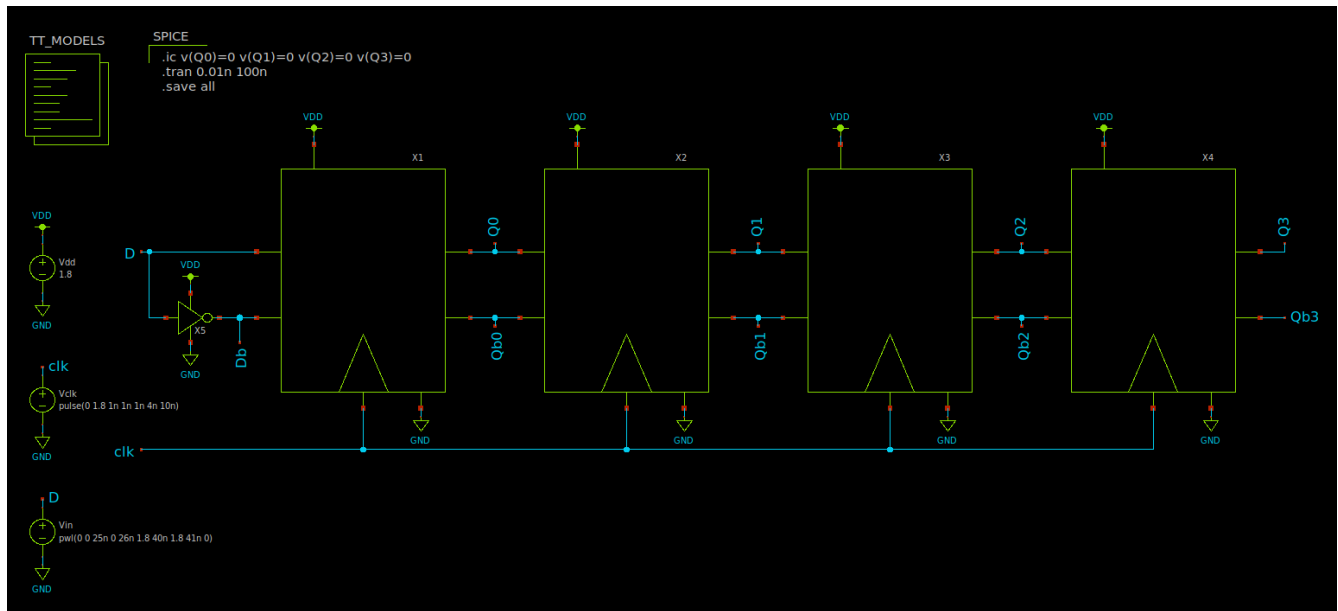


Figure 5: Test harness schematic for 4-bit shift register.

This simulation produced the waveforms shown in Figure 5. I was initially alarmed that the  $Q_{(0-3)}$  rising edges did not reach the full 1.8 V, but after asking Brad I learned that this is because the CSRL latch can only pass one logic value strongly due to the type of the pass transistors.

 


Figure 5: Waveforms for shift register transient simulation.

Once I had verified that my schematic worked, I implemented the shift register layout by importing four instances of the CSRL latch and one inverter cell as shown in Figure 6.

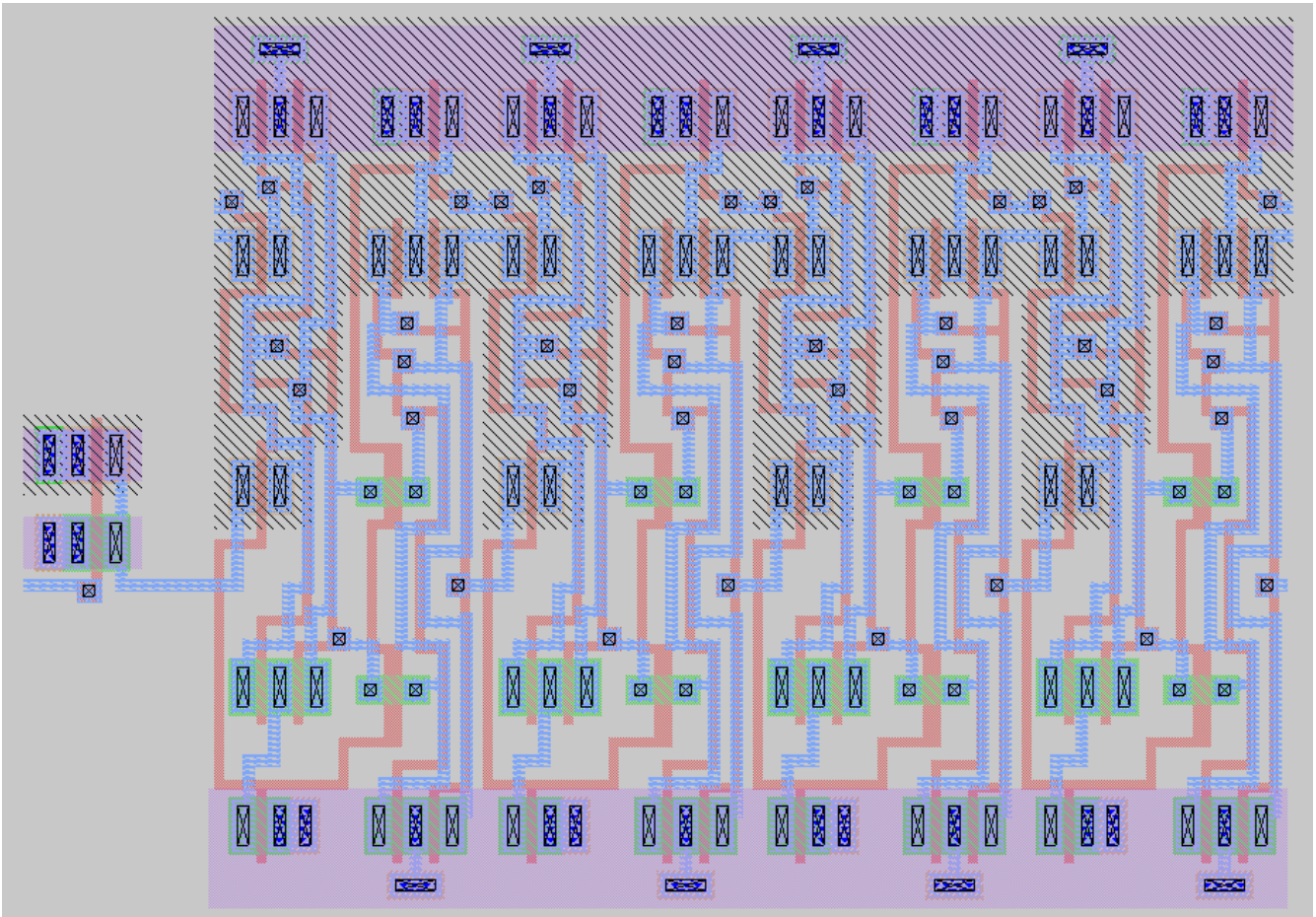


Figure 6: Shift register layout.

I probably could have edited my inverter to make it narrower, but I just ended up using the inverter from Miniproject 1.

I performed LVS on the shift register to ensure that the netlists matched which they did. The output file is in the *Shift\_reg/lvs/* folder.

\*\*\*